SYNTHETIC BROWSER WORKFLOW CHECK

CAT II - Digital Electronics - 100 marks

Question 1: Explain a digital circuit. (100 marks)